

# Protokol Skříňka

## Zadání:

Navrhněte Mealyho automat, který řeší otevírání skříňky na vlakovém nádraží. Cena je 5Kč, vhazované mince jsou 1,2 a 5-koruna. Automat vrácí 1Kč pouze v případě, že zákazník vhodil 4Kč a následně 2-korunovou minci. Výstupy, jestli se skříňka otevře, nebo vrátí i peníze, se budou zobrazovat na LED diodách.

## Teoretický rozbor Spartan a VHDL:

Spartan je programovatelné hradlové pole, což je typ logického integrovaného obvodu, který je vyroben tak, aby mohl být naprogramován kdykoliv. Obsahuje pole programovatelných logických obvodů (PLD), logických bloků, umožňuje je navzájem propojit a tím vytvořit takřka libovolné číslicové zařízení. Mikroprocesor je víceúčelové programovatelné zařízení, které na vstupu akceptuje digitální data, zpracuje je pomocí instrukcí uložených v paměti a jako výstup zobrazí výsledek. Mikroprocesor představuje příklad sekvenčního logického obvodu, který pro uložení dat používá dvojkovou soustavu.

VHDL je programovací jazyk, který slouží pro popis hardwaru. Používá se pro návrh a simulaci digitálních integrovaných obvodů, například programovatelných hradlových polí nebo různých zákaznických obvodů. Umožňuje návrh jak logických tak i sekvenčních struktur a jeho hlavní výhodou je jeho univerzálnost.

## Definice stavů a jejich kódování:

		btn0	btn1	btn2
X0	(0 Kč)	0	0	0
X1	(1 Kč)	1	0	0
X2	(2 Kč)	0	1	0
X3	(5 Kč)	0	0	1

Vstupní proměnné:

	q2	q1	q0
S0	0	0	0
S1	0	0	1
S2	0	1	0
S3	0	1	1
S4	1	0	0

Vnitřní proměnné:


	S0	S1
Y0	0	0
Y1	1	0
Y2	1	1

Výstupní proměnné:

### Popis automatu Mealy:

Mealyho automat se označuje jako konečný automat s výstupem. Výstup je generován na základě příchozího vstupu i momentálního stavu. Jeho stavový diagram automatu má ke každému přechodu přiřazenu nejen vstupní hodnotu, kterou je přechod aktivován, ale i výstupní hodnotu, která je při aktivaci přechodu vygenerována.

### Orientovaný graf:

 

Tabulky přechodů mezi vnitřními stavy v závislosti na vstupních stavech, tabulky výstupů:

	$X0/Y$	$X1/Y$	$X2/Y$	$X3/Y$
S0	S0/Y0	S1/Y0	S2/Y0	S0/Y1
S1	S1/Y0	S2/Y0	S3/Y0	S0/Y1
S2	S2/Y0	S3/Y0	S4/Y0	S0/Y1
S3	S3/Y0	S4/Y0	S0/Y1	S0/Y1
S4	S4/Y0	S0/Y1	S0/Y2	S0/Y1

## VHDL moduly – programy:

Dělička:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity delicka is
7      Port ( CLK_in : in  STD_LOGIC;
8            CLK_out : out STD_LOGIC);
9  end delicka;
10
11 architecture Behavioral of delicka is
12
13 begin
14
15     process (CLK_in)
16         variable i : integer range 0 to 15000000 ;
17     begin
18         if rising_edge(CLK_in) then
19             if i=0 then CLK_out <= '1' ;
20                 i := 9843000 ;
21             else
22                 CLK_out <= '0' ;
23                 i := i - 1 ;
24             end if ;
25         end if ;
26     end process;
27
28 end Behavioral;
```

Dekodér:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4
5
6  entity dekoder is
7      Port ( HEX : in  STD_LOGIC_VECTOR (2 downto 0);
8            LED : out STD_LOGIC_VECTOR (6 downto 0)
9            );
10 end dekoder;
11
12
13 architecture Behavioral of dekoder is
14
15 begin
16
17
18     with HEX SElect
19     LED<= "1111001" when "0001",  --1
20           "0100100" when "0010",  --2
21           "0110000" when "0011",  --3
22           "0011001" when "0100",  --4
23           "1000000" when others;  --0
24
25 end Behavioral;
```

Skříňka:


```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4
5  entity automat1 is
6      Port (
7          clk : in  STD_LOGIC;
8          rst : in  STD_LOGIC;
9          mince : in  STD_LOGIC_VECTOR (2 downto 0);
10         vyst : out STD_LOGIC_VECTOR (1 downto 0);
11         stavy : out STD_LOGIC_VECTOR (2 downto 0));
12 end automat1;
13
14 architecture Behavioral of automat1 is
15     signal state, next_state : STD_LOGIC_VECTOR (2 downto 0);
16
17     constant s0 : STD_LOGIC_VECTOR (2 downto 0) := "000";
18     constant s1 : STD_LOGIC_VECTOR (2 downto 0) := "001";
19     constant s2 : STD_LOGIC_VECTOR (2 downto 0) := "010";
20     constant s3 : STD_LOGIC_VECTOR (2 downto 0) := "011";
21     constant s4 : STD_LOGIC_VECTOR (2 downto 0) := "100";
22
23 begin
24
25     SYNC_PROC: process (clk)
26     begin
27         if rising_edge (clk)
28             then if (rst='0')
29                 then state <= next_state;
30                 else state <= s0;
31             end if;
32         end if;
33     end process SYNC_PROC;
34
35
36
37     OUTPUT_DECODE: process (mince)
38     begin
39
40         case (state) is
41             when s0 =>
42                 if (mince = "000") then vyst <= "00";
43                 elsif (mince = "100") then vyst <= "00";
44                 elsif (mince = "010") then vyst <= "00";
45                 elsif (mince = "001") then vyst <= "10";
46                 else vyst <= "00";
47                 end if;
48             when s1 =>
49                 if (mince = "000") then vyst <= "00";
50                 elsif (mince = "100") then vyst <= "00";
51                 elsif (mince = "010") then vyst <= "00";
52                 elsif (mince = "001") then vyst <= "10";
53                 else vyst <= "00";
54                 end if;
55             when s2 =>
56                 if (mince = "000") then vyst <= "00";
57                 elsif (mince = "100") then vyst <= "00";
58                 elsif (mince = "010") then vyst <= "00";
59                 elsif (mince = "001") then vyst <= "10";
60                 else vyst <= "00";
61                 end if;
62             when s3 =>
63                 if (mince = "000") then vyst <= "00";
64                 elsif (mince = "100") then vyst <= "00";
65                 elsif (mince = "010") then vyst <= "10";
66                 elsif (mince = "001") then vyst <= "10";
67                 else vyst <= "00";
68                 end if;
69             when s4 =>
70                 if (mince = "000") then vyst <= "00";
71                 elsif (mince = "100") then vyst <= "10";
72                 elsif (mince = "010") then vyst <= "11";
73                 elsif (mince = "001") then vyst <= "10";
74                 else vyst <= "00";
75                 end if;
76
77             when others => NULL;
78         end case;
79
80     end process OUTPUT_DECODE;
81
82
83     NEXT_STATE_DECODE: process (state, mince)
84     begin
85
86         case (state) is
87             when s0 =>
88                 if (mince = "000") then next_state <= s0; stavy <="000";
```

```


89         elsif (mince = "100") then next_state <= s1; stavy <="001";
90         elsif (mince = "010") then next_state <= s2; stavy <="010";
91         elsif (mince = "001") then next_state <= s0; stavy <="000";
92             else next_state <= s0;
93         end if;
94
95     when s1 =>
96         if (mince = "000") then next_state <= s1; stavy <="001";
97         elsif (mince = "100") then next_state <= s2; stavy <="010";
98         elsif (mince = "010") then next_state <= s3; stavy <="011";
99         elsif (mince = "001") then next_state <= s0; stavy <="000";
100             else next_state <= s1;
101         end if;
102
103     when s2 =>
104         if (mince = "000") then next_state <= s2; stavy <="010";
105         elsif (mince = "100") then next_state <= s3; stavy <="011";
106         elsif (mince = "010") then next_state <= s4; stavy <="100";
107         elsif (mince = "001") then next_state <= s0; stavy <="000";
108             else next_state <= s2;
109         end if;
110
111     when s3 =>
112         if (mince = "000") then next_state <= s3; stavy <="011";
113         elsif (mince = "100") then next_state <= s4; stavy <="100";
114         elsif (mince = "010") then next_state <= s0; stavy <="000";
115         elsif (mince = "001") then next_state <= s0; stavy <="000";
116             else next_state <= s3;
117         end if;
118
119     when s4 =>
120         if (mince = "000") then next_state <= s4; stavy <="100";
121         elsif (mince = "100") then next_state <= s0; stavy <="000";
122         elsif (mince = "010") then next_state <= s0; stavy <="000";
123         elsif (mince = "001") then next_state <= s0; stavy <="000";
124             else next_state <= s4;
125         end if;
126
127 when others => NULL;
128 end case;
129 stavy <= state;
130
131 end process NEXT_STATE_DECODE;
132
133
134
135 end Behavioral;
136

```

Simulace:

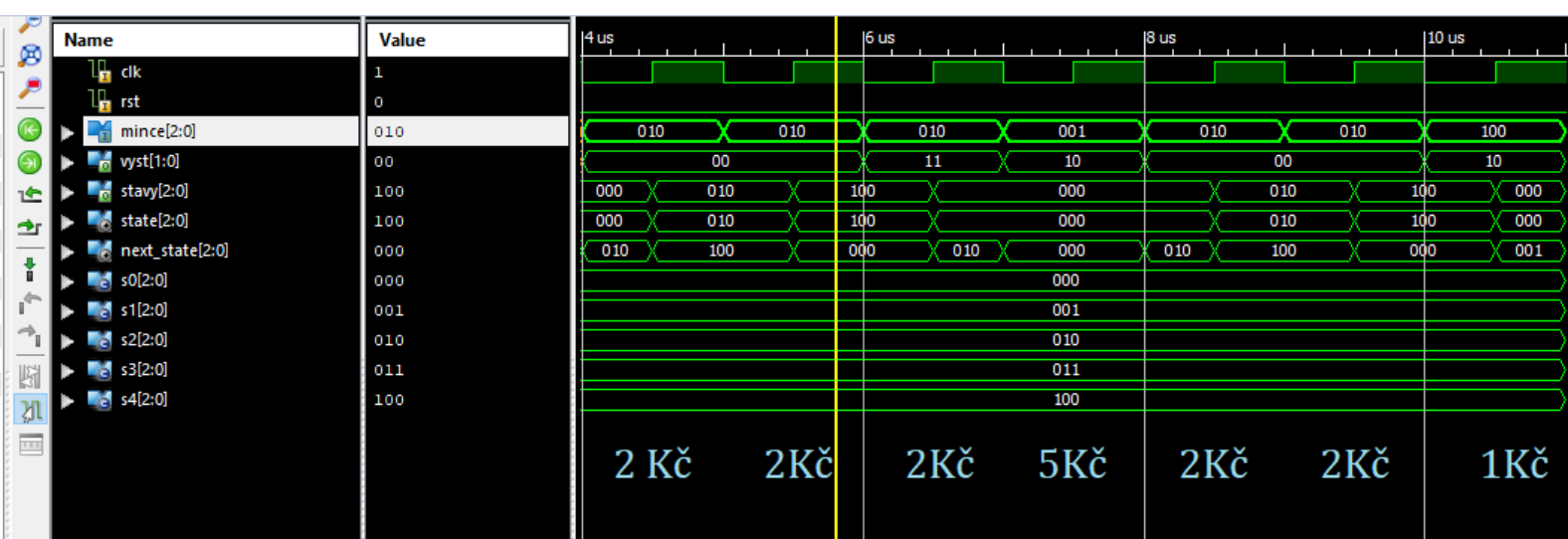

## Schéma:

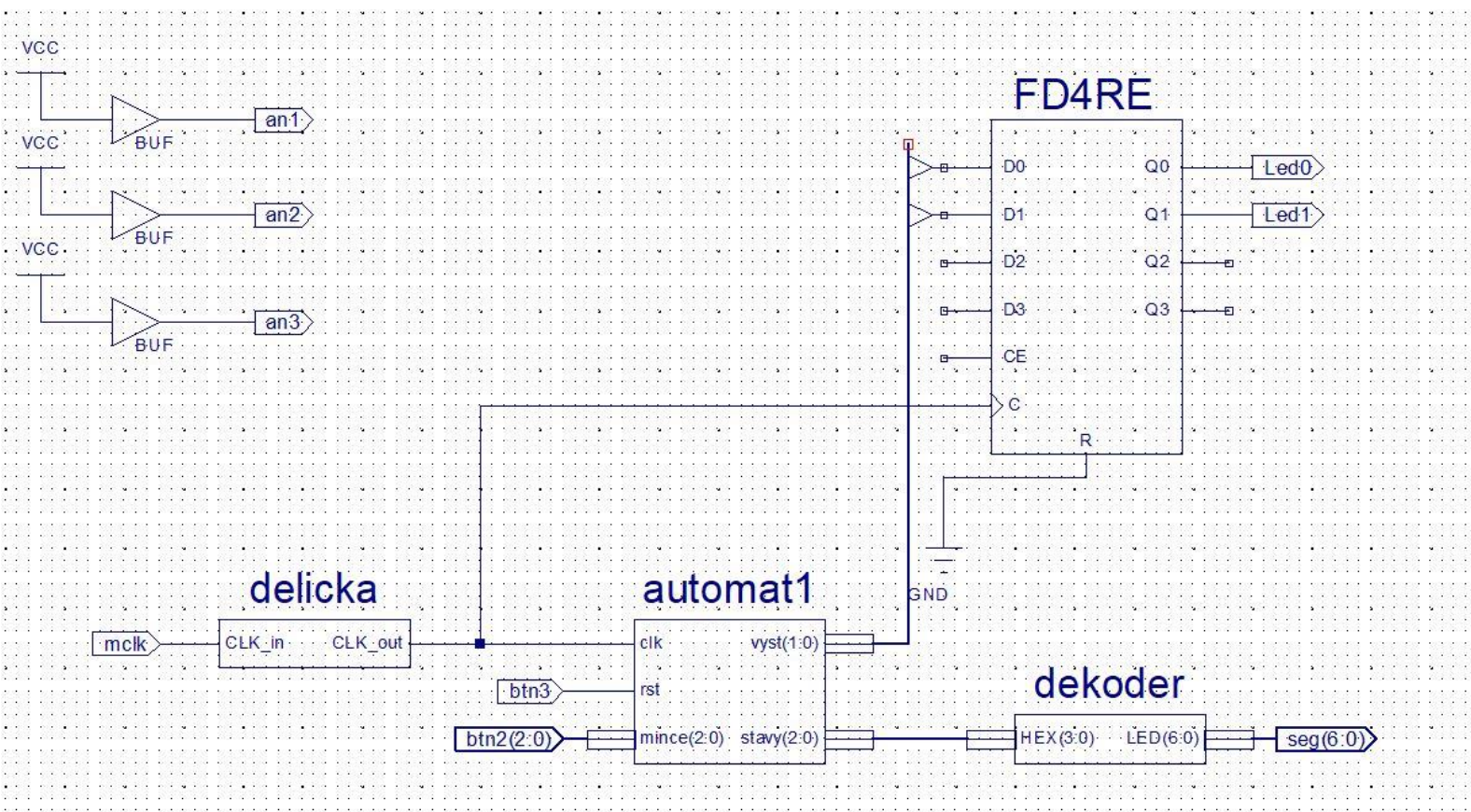

## Piny:

```
# clock pins for Basys2 Board
NET "mclk" LOC = "B8"; # Bank = 0, Signal name = MCLK

# Pin assignment for DispCtl
# Connected to Basys2 onBoard 7seg display
NET "seg<0>" LOC = "L14"; # Bank = 1, Signal name = CA
NET "seg<1>" LOC = "H12"; # Bank = 1, Signal name = CB
NET "seg<2>" LOC = "N14"; # Bank = 1, Signal name = CC
NET "seg<3>" LOC = "N11"; # Bank = 2, Signal name = CD
NET "seg<4>" LOC = "P12"; # Bank = 2, Signal name = CE
NET "seg<5>" LOC = "L13"; # Bank = 1, Signal name = CF
NET "seg<6>" LOC = "M12"; # Bank = 1, Signal name = CG
#NET "dp" LOC = "N13"; # Bank = 1, Signal name = DP

NET "an3" LOC = "K14"; # Bank = 1, Signal name = AN3
NET "an2" LOC = "M13"; # Bank = 1, Signal name = AN2
NET "an1" LOC = "J12"; # Bank = 1, Signal name = AN1
#NET "an0" LOC = "F12"; # Bank = 1, Signal name = AN0

# Pin assignment for LEDs
#NET "Led<7>" LOC = "G1" ; # Bank = 3, Signal name = LD7
#NET "Led<6>" LOC = "P4" ; # Bank = 2, Signal name = LD6
#NET "Led<5>" LOC = "N4" ; # Bank = 2, Signal name = LD5
#NET "Led<4>" LOC = "N5" ; # Bank = 2, Signal name = LD4
#NET "Led<3>" LOC = "P6" ; # Bank = 2, Signal name = LD3
#NET "Led<2>" LOC = "P7" ; # Bank = 3, Signal name = LD2
NET "Led<1>" LOC = "M11" ; # Bank = 2, Signal name = LD1
NET "Led0" LOC = "M5" ; # Bank = 2, Signal name = LD0

# Pin assignment for SWs
#NET "sw7" LOC = "N3"; # Bank = 2, Signal name = SW7
#NET "sw6" LOC = "E2"; # Bank = 3, Signal name = SW6
#NET "sw5" LOC = "F3"; # Bank = 3, Signal name = SW5
#NET "sw4" LOC = "G3"; # Bank = 3, Signal name = SW4
#NET "sw3" LOC = "B4"; # Bank = 3, Signal name = SW3
#NET "sw2" LOC = "K3"; # Bank = 3, Signal name = SW2
#NET "sw1" LOC = "L3"; # Bank = 3, Signal name = SW1
#NET "sw0" LOC = "P11"; # Bank = 2, Signal name = SW0

NET "btn3" LOC = "A7"; # Bank = 1, Signal name = BTN3
NET "btn<2>" LOC = "M4"; # Bank = 0, Signal name = BTN2
NET "btn<1>" LOC = "C11"; # Bank = 2, Signal name = BTN1
NET "btn<0>" LOC = "G12"; # Bank = 0, Signal name = BTN0

## Pin assignment for PS2
#NET "ps2c" LOC = "B1" | DRIVE = 2 | PULLUP ; # Bank = 3, Signal name = PS2C
#NET "ps2d" LOC = "C3" | DRIVE = 2 | PULLUP ; # Bank = 3, Signal name = PS2D
```

## Zhodnocení:

Úkolem bylo vytvořit funkční skříňku, která se bude otevírat a otevírat i vracet korunu podle toho, kolik jsme vložili korun do skříňky. Budou se nám rozsvícovat ledky podle našich výstupů. S tímto úkolem jsem měl problém, kvůli kterému se mi skříňka otevírala předem, naštěstí jsem měl pouze špatně nastavený clock. Program jsme celý dělali doma a byl celkem obtížný.